

Programming Assignment #2: AC CIRCUIT ANALYSIS

It is useful to be able to generate tables of information involving repeated calculations in engineering. One example of this is where the current is to be calculated (as a function of frequency) for a series RLC electrical circuit.

Background:

Shown on page 3 is a "series RLC" circuit, consisting of a sinusoidal voltage source, a resistor, an inductor, and a capacitor. The current I in this circuit changes as the frequency of the sinusoidal voltage changes.

R = Resistance in Ohms (Ω)

L = Inductance in Henries (H)

C = Capacitance in Farads (F)

I = Current in Amperes (A)

E = Sinusoidal voltage in Volts (V), at some frequency, f

f = Frequency in Hertz (Hz)

The current, I , can be calculated in the circuit using the following relationships:

$$X_L = \text{inductive reactance} = 2 \cdot \pi \cdot f \cdot L \text{ in ohms } (\Omega)$$

$$X_C = \text{capacitive reactance} = \frac{-1}{2 \cdot \pi \cdot f \cdot C} \text{ in ohms } (\Omega)$$

$$Z = \text{total circuit impedance} = \sqrt{R^2 + (X_L + X_C)^2} \text{ in Ohms } (\Omega)$$

$$I = \text{current} = \frac{E}{Z} \text{ in Amperes (A)}$$

Program Requirements:

1. The user should be prompted to input the values for E , R , L , C , f_{initial} and f_{final} .
 - The value for R should be entered in ohms (for example, the user enters 5000.)
 - The value of E should be entered in volts
 - The value of C should be entered in mF, uF, or nF (then convert it to F). For example, the user enters 10 mF.
 - The value of L should be entered in mH or uH (then convert it to H).
 - The value of f_{initial} should be entered in Hz, kHz, or MHz (then convert it to Hz).
2. Create a table containing values of f , X_L , X_C , Z , and I for a range of values of f .
 - Use a loop vary f from f_{initial} to the first value of f greater than or equal to f_{final} where f doubles each time through the loop. For example, if $f_{\text{initial}} = 100$ and $f_{\text{final}} = 1\text{E}6$, then $f = 100, 200, 400, 800, \dots, 1638400$ (this spacing is common as graphs often place frequency on a log scale).
 - During each pass through the loop call separate functions to calculate X_L , X_C , and Z .
 - Use at least two additional functions.

- The results should be displayed in a neat, formatted table with headings, units, etc. The value of the current, I, should be printed in mA rather than Amperes. An example of what this table might look like is shown below. The lines in the table are not required.
 - Your loop should also determine the maximum value of the current in the table and the corresponding frequency.
3. The output should be the table described above, as well as a title or brief explanation of the program, the values of the inputs, and the maximum value of the current and the frequency where I is maximum (include units with all input and output values).
 4. The results should display f as an integer; XC, XL, and Z using one digit after the decimal point; and I with 3 digits after the decimal point (as shown below). The numbers should not be printed in scientific notation.
 5. Include a loop that will give the user the option of re-running the program.
 6. Include loops to allow the user to correct bad inputs. Test for the following:
 - Values entered for R, L, C, and E must be positive.
 - Proper units and prefixes must be used with inputs as described above.
 - $f_{\text{initial}} \geq 1 \text{ Hz}$, $f_{\text{final}} \leq 1\text{E}9 \text{ Hz}$, and $f_{\text{final}} > 2*f_{\text{initial}}$.

Example Output Table: (for $R = 5000 \Omega$, $L = 20 \text{ mH}$, $C = 0.02 \mu\text{F}$, $E = 15\text{V}$, $f_{\text{initial}} = 100$, and $f_{\text{final}} = 1\text{E}6$). Note: You might be able to print the ohm (Ω) symbol using the ASCII extended character set (cout << "10M\352"; - to print 10 M Ω).

Freq (Hz)	XC (Ω)	XL (Ω)	Z (Ω)	I (mA)
100	-79577.5	12.6	79721.9	0.188
200	-40000.5	25.1	40286.4	0.372
.
.
.
1638400	-4.9	205887.4	205943.3	0.073

Program Testing: Print your results and include them with your report for the following two cases:

- 1) The example shown above.
- 2) The values shown corresponding to your name in the table on the following page.

Extra Credit Suggestions: (up to 10 additional points)

1. Use prefixes to display the values of XC, XL, and Z in the output table as follows:
 - if value < 1000 - express in Ohms (Ω)
 - if $1000 \leq \text{value} < 1000000$ - express in kiloOhms (k Ω)
 - if value ≥ 1000000 - express in MegaOhms (M Ω)
2. Express the frequency in Hz, kHz, and MHz (like suggestion 2 above).
3. Instead of suggestion 3 above, use commas in expressing the frequency (e.g., 80,000 instead of 80000).
4. Send the information from your table to a data file and retrieve the data and graph R, XL, XC, and Z versus frequency using Excel.
5. Create and use a library containing all of your functions.
6. Use your imagination!

Table 1: Input values

Name	R (Ω)	L (mH)	C (μ F)	E (V)	f _{initial} (Hz)	f _{final} (Hz)
Ash	1000	6.33	1.0	48	50	1E5
Babcock	1500	1.76	0.9	47	100	2E5
Bagley	2200	0.49	0.8	46	200	3E5
Barnet	2700	25.3	0.01	45	250	4E5
Campbell	3300	3.17	0.02	44	300	5E5
Chen	3900	1.58	0.01	43	350	8E5
Diop	4700	0.79	0.005	42	400	1E6
Harris	1000	3.96	0.9	41	500	2E6
Holterhaus	1500	13.2	0.8	40	550	3E6
Ivanov	2200	31.7	0.01	39	600	4E6
Knust	2700	12.7	0.02	38	650	5E6
Lewis	3300	15.8	0.01	37	700	8E6
Mann	3900	1.98	0.005	36	750	2E6
Mayo	4700	2.53	0.002	35	800	3E6
McDougal	5600	12.7	0.9	34	850	4E6
McDowell	5600	1.27	0.002	33	450	5E6
Noffsinger	6200	7.04	0.9	32	500	8E6
Paz	6800	3.96	0.4	31	550	4E6
Pham	8200	13.2	0.03	30	600	5E6
Quiatchon	9100	31.7	0.008	29	650	8E6
Ryser	8200	12.7	0.005	28	700	1E7
Tendilla	6800	15.8	0.001	27	750	2E7
Tmara	6200	1.98	0.002	26	800	3E7
Van Dam	5600	2.53	0.001	25	850	4E7
Vanta	4700	12.7	0.5	24	900	5E7
	3900	15.8	0.1	23	950	8E7

Series RLC Circuit: